

Métodos Experimentais em Física dos Materiais – FMT2501

2º Semestre de 2009

Instituto de Física
Universidade de São Paulo

Professor: **Antonio Domingues dos Santos**

E-mail: adsantos@if.usp.br


Fone: 3091.6886

Entrada diferencial

Wikipedia:

An instrumentation (or instrumentational) amplifier is a type of [differential amplifier](#) that has been outfitted with input buffers, which eliminate the need for input impedance matching and thus make the amplifier particularly suitable for use in measurement and [test equipment](#).

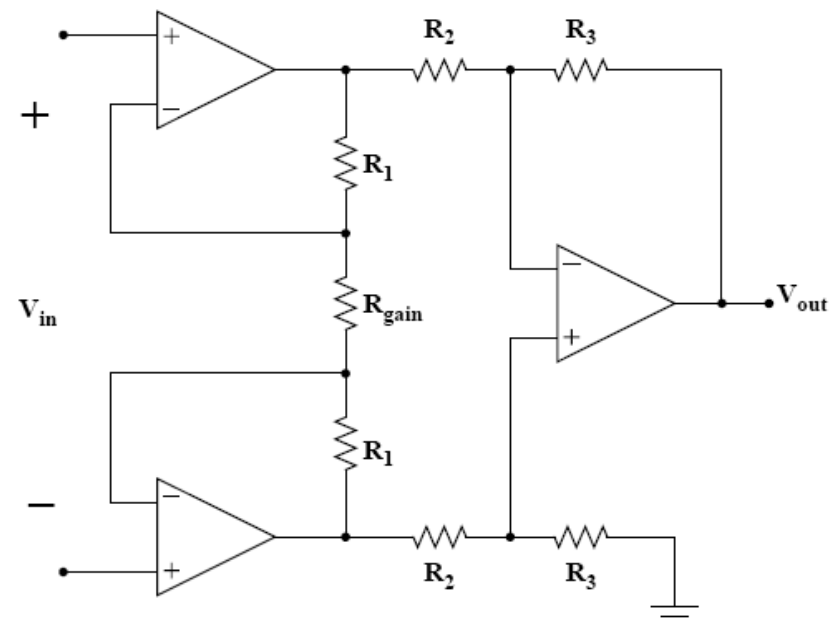
Additional characteristics include very low [DC offset](#), low [drift](#), low [noise](#), very high [open-loop gain](#), very high [common-mode rejection ratio](#), and very high [input impedances](#). Instrumentation amplifiers are used where great [accuracy](#) and [stability](#) of the [circuit](#) both short- and long-term are required.



$$\frac{V_{out}}{V_2 - V_1} = \left(1 + \frac{2R_1}{R_{gain}}\right) \frac{R_3}{R_2}$$

Entrada diferencial

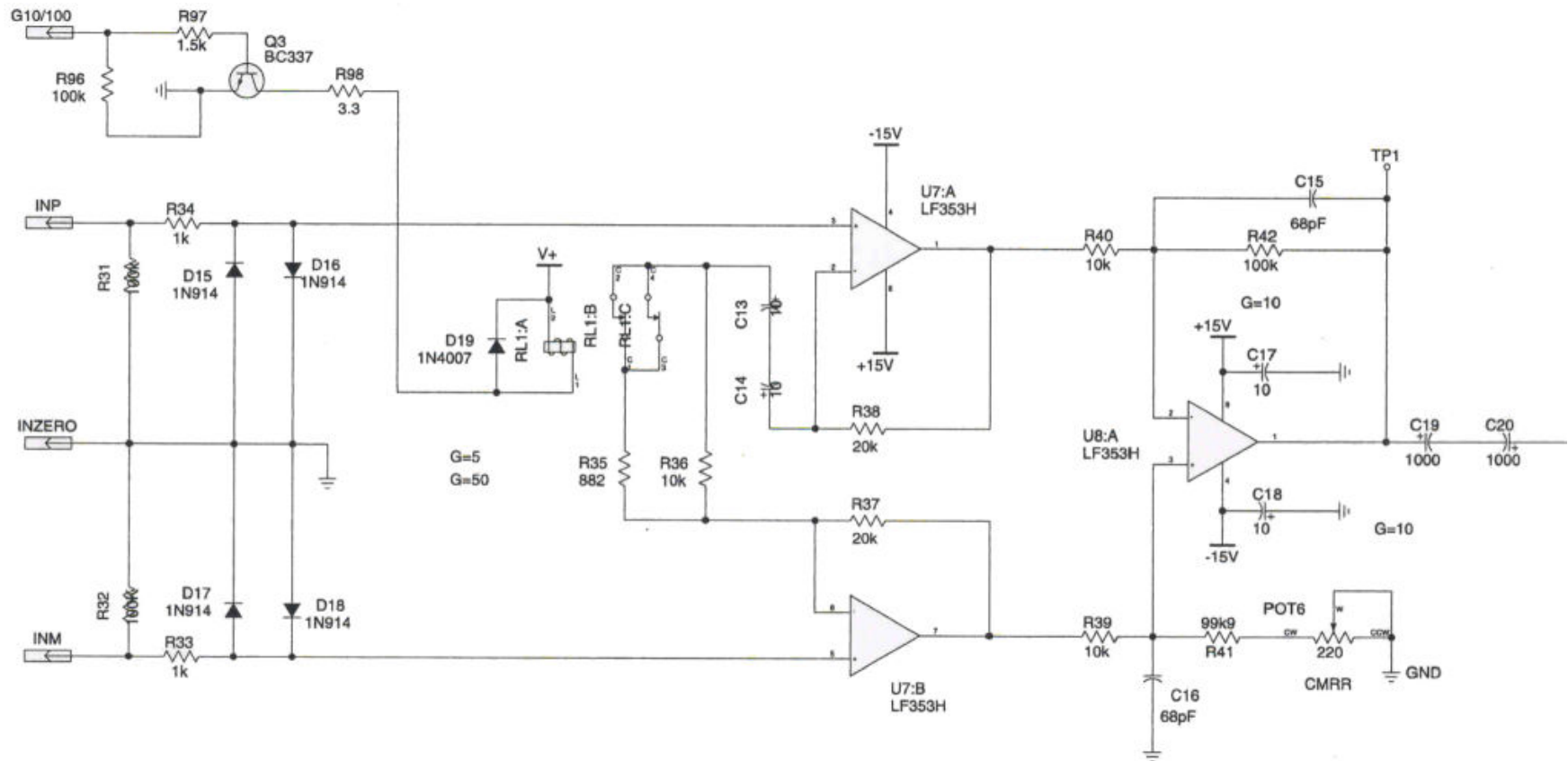
$$\frac{V_{out}}{V_2 - V_1} = \left(1 + \frac{2R_1}{R_{gain}}\right) \frac{R_3}{R_2}$$



Resposta em frequência (vista espectral)

$$v = \frac{4A}{\pi} \sum_{n=\text{impar}} \frac{\sin(2\pi n f_0 t)}{n}$$


Filtro passa-baixas

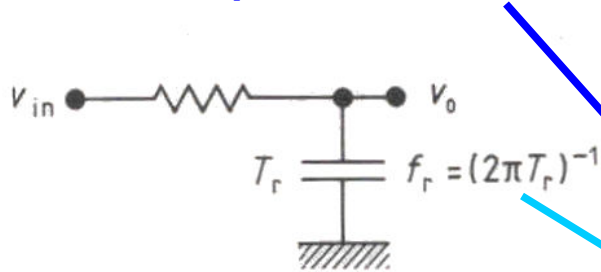

Para um sinal non-senoidal
de frequência f_0


(série de Fourier)
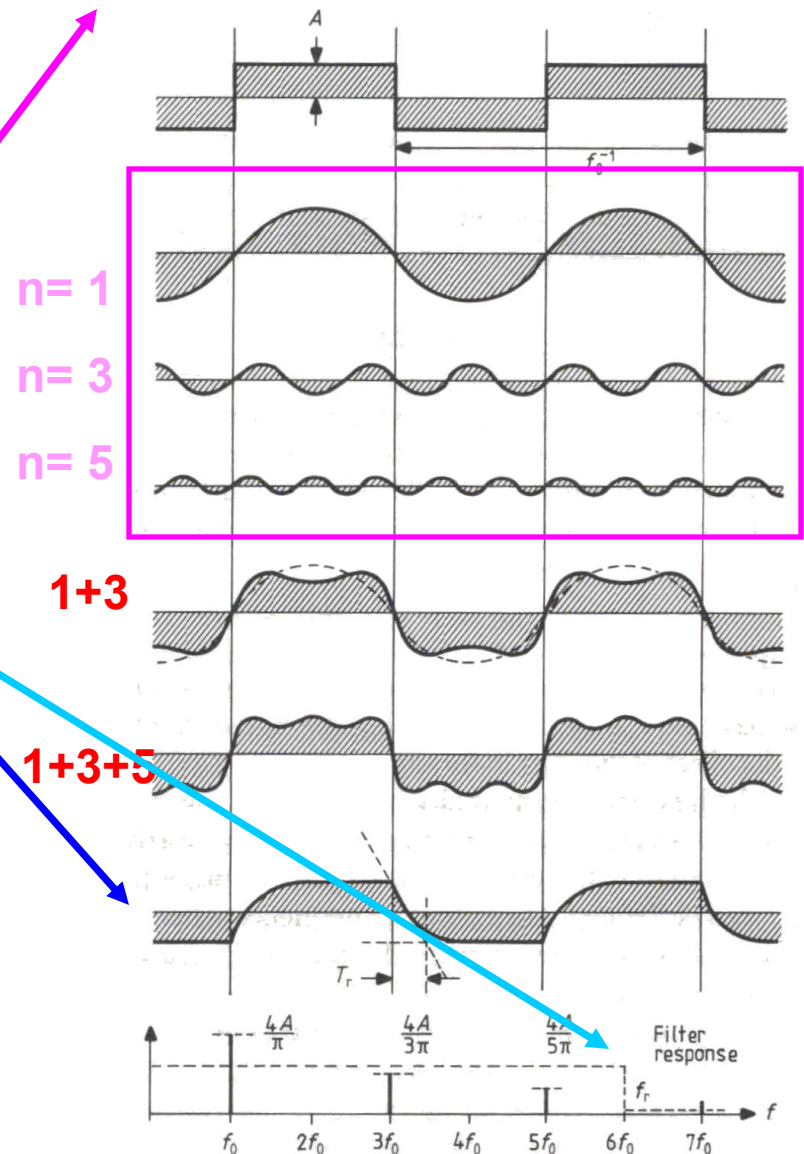
$$v = A_0 + \sum_{n=1}^{\infty} [A_n \cos(2\pi n f_0 t) + B_n \sin(2\pi n f_0 t)]$$



Resposta em frequência (vista espectral)

Filtro passa-baixas

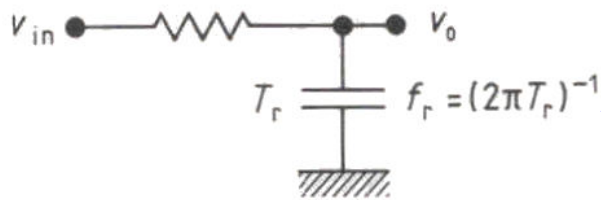


$$V_c = v_{0c} \exp[j(2\pi ft + \phi_c)]$$

$$I_c = C \frac{dV_c}{dt} = j2\pi fCV_c$$

$$\therefore Z_c = \frac{V_c}{I_c} = \frac{1}{j2\pi fC} = \frac{1}{j\omega C}$$

$$V = v_0 \exp[j(2\pi ft + \phi)] = v_0 \cos(2\pi ft + \phi) + jv_0 \sin(2\pi ft + \phi)$$

Fasor

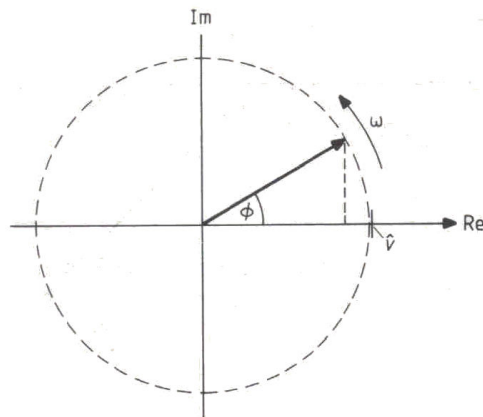

Phasor representation of $V = \hat{v} \exp[j(\omega t + \phi)]$

$$V_{in} = (R + Z_c)I$$


$$V_{out} = Z_c I$$

$$\therefore V_{out} = \frac{Z_c}{R + Z_c} V_{in}$$

$$V_{out} = \frac{1}{1 + j\omega / \omega_r} V_{in}$$

Resposta em frequência (vista espectral)


Filtro passa-baixas

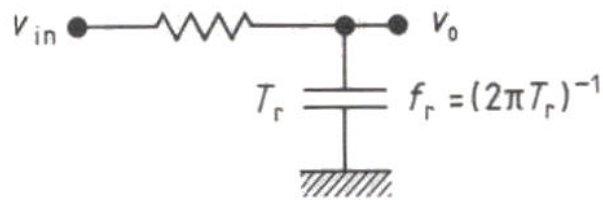

$$V_{out} = \frac{1}{1 + j\omega / \omega_r} V_{in}$$


$$V_{out} = T_r^{-1} \int_{t-T_r}^t v_{in} \exp(j\omega t') dt'$$
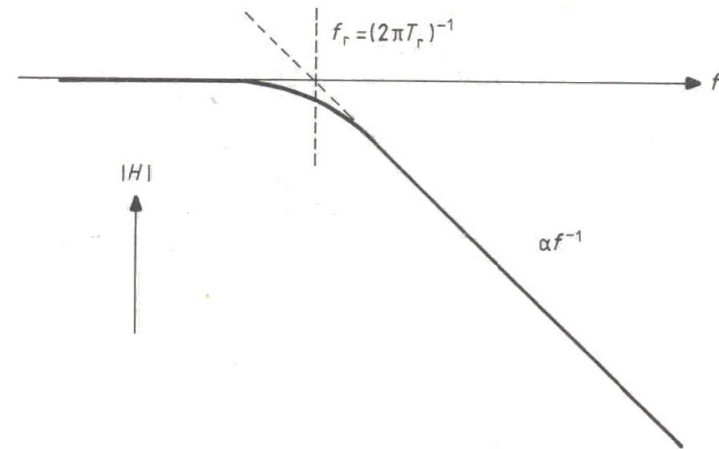
$$V_{out} = V_{in}(t) \exp(-j\omega T_r / 2) \frac{\sin(\omega T_r)}{\omega T_r / 2}$$



Resposta em frequência (vista espectral)

Filtro passa-baixas

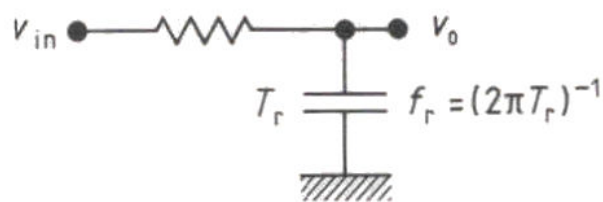

$$V_{out} = T_r^{-1} \int_{t-T_r}^t v_{in} \exp(j\omega t') dt'$$

$$V_{out} = V_{in}(t) \exp(-j\omega T_r / 2) \frac{\sin(\omega T_r)}{\omega T_r / 2}$$

